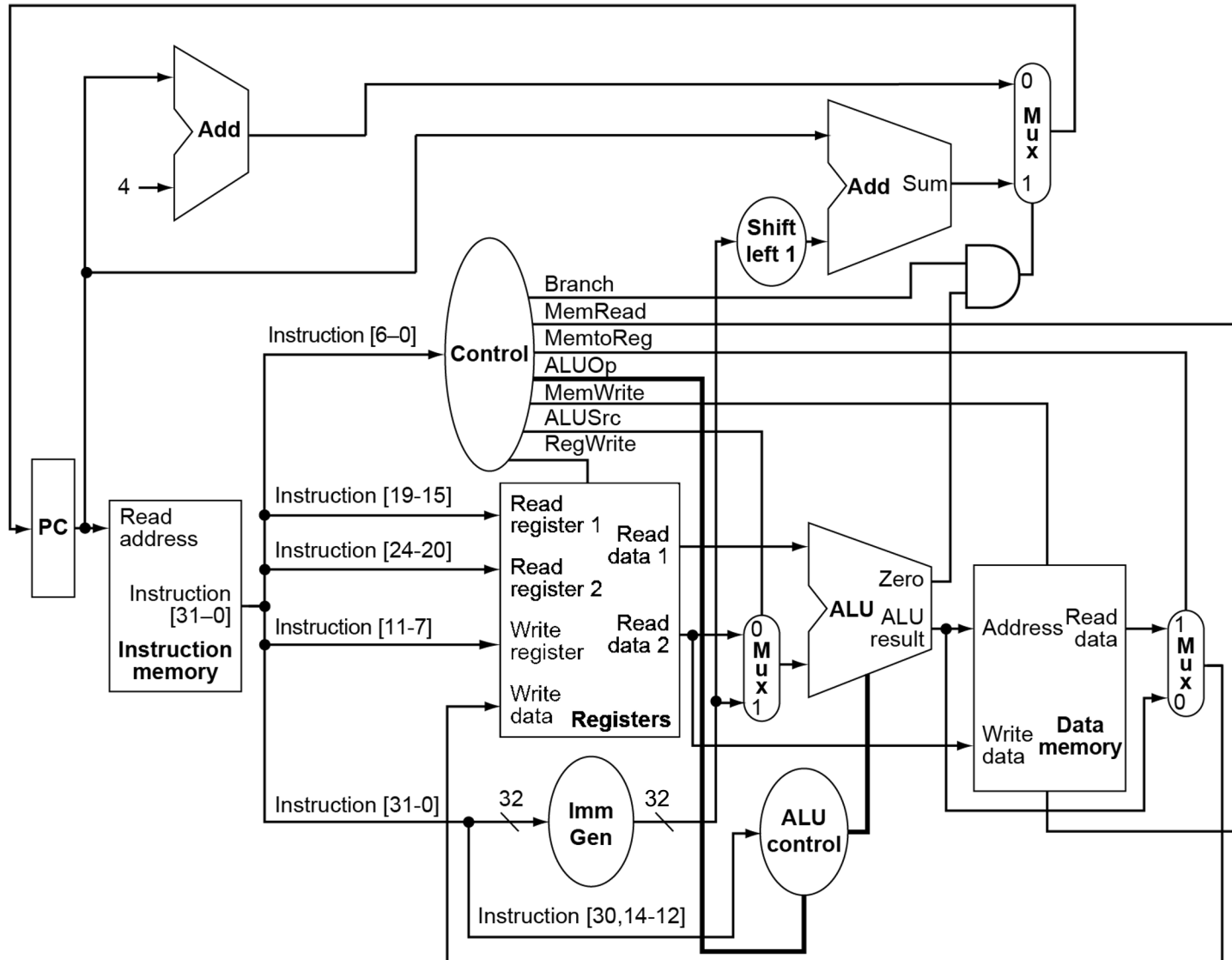


# **Topic 6**


---

## **Pipelined Processor**

# Single Cycle Implementation




# Single Cycle Implementation

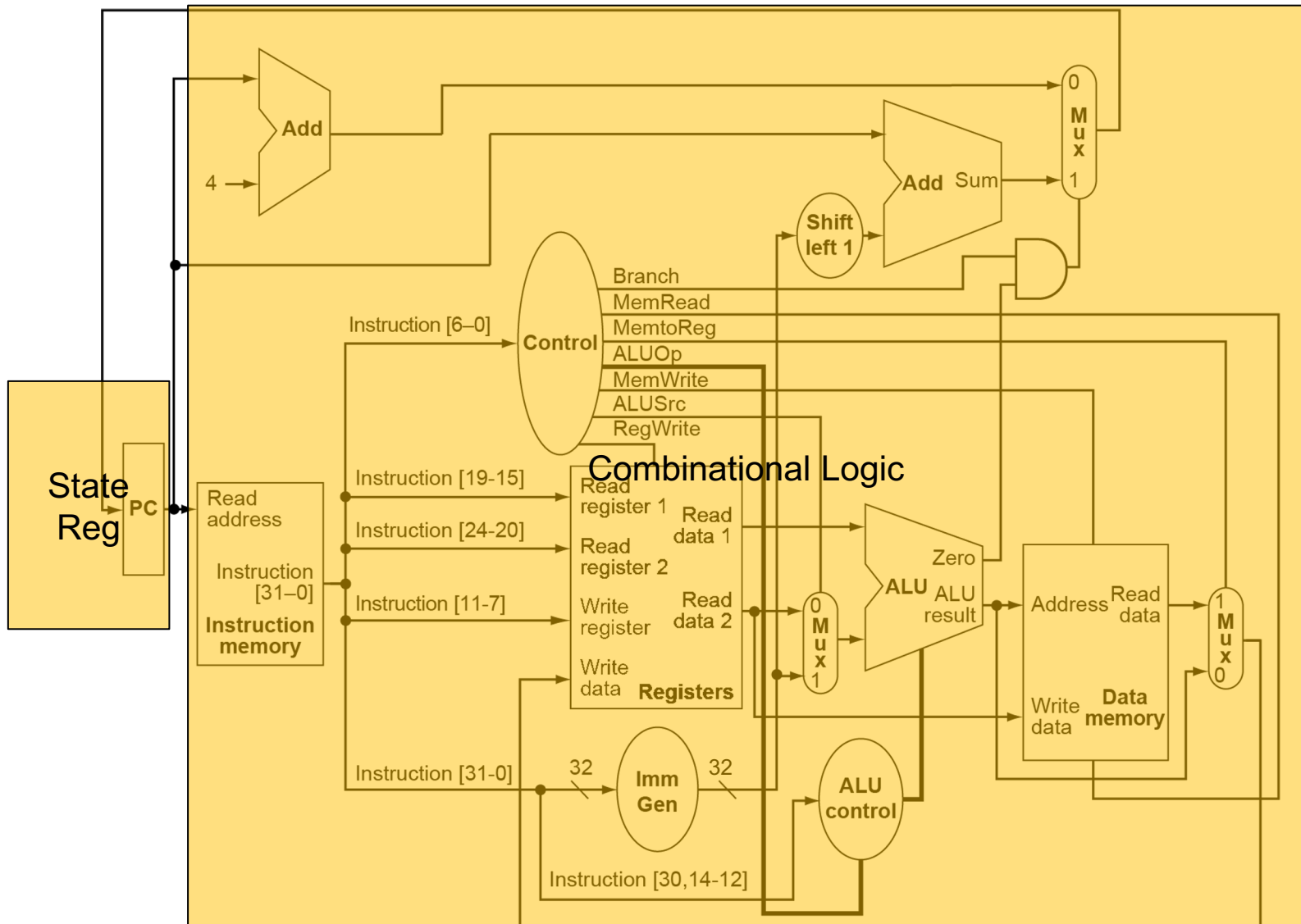



# State Machine

- Finite State Machine

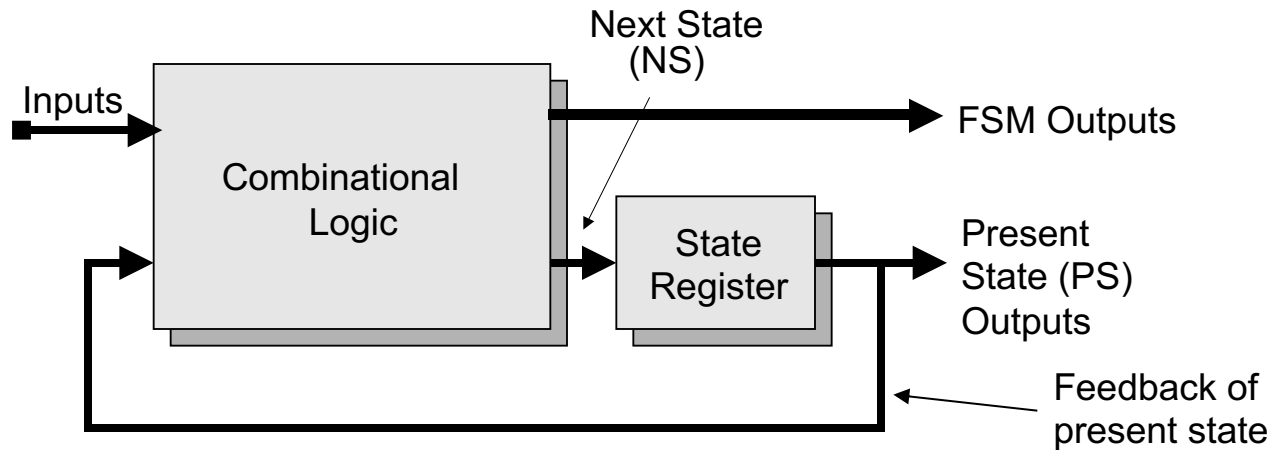
  
# Clocking Methodology

- Combinational logic does the computation during clock cycles
  - Between clock edges
  - Input (present state) from state elements, output (next state) to state element
  - Among all kinds of computations, longest delay determines clock period



# Performance Consideration

- Longest instruction determines the clock cycle time
  - Critical path: the path having longest delay
    - load instruction  
Instruction memory → register file → ALU → data memory → register file (plus MUXes)
- Not feasible to vary period for different instructions
  - Waste time on other instructions
- How to improve the performance (faster speed)?

# Performance Consideration

- Assume times for major components are
  - 100ps for register read or write
  - 200ps for accessing memory
  - 200ps for ALU operations

Instruction	Instr fetch	Register read	ALU op	Data Memory	Register write	Total time
lw	200ps	100 ps	200ps	200ps	100 ps	800ps
sw	200ps	100 ps	200ps	200ps		700ps
R-format	200ps	100 ps	200ps		100 ps	600ps
beq	200ps	100 ps	200ps			500ps


# Performance Consideration

- Assume 100 instructions are executed
  - 15% are loads
  - 15% are stores
  - 40% are R format instructions
  - 30% are branches
- What's the clock cycle time for single-cycle processor?
- Execution time using single-cycle processor?



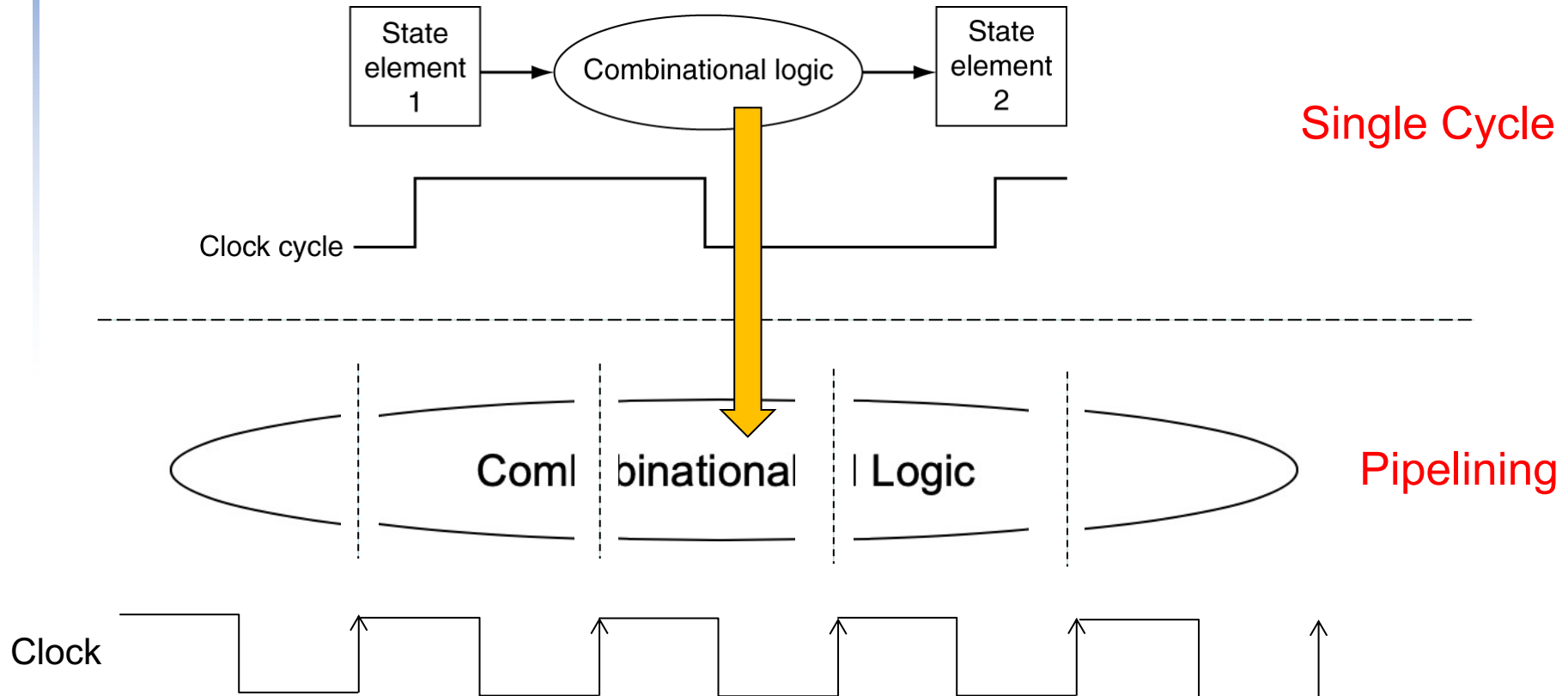
# Improvement – Pipelining

- Divide the combinational logic into smaller pieces



- Each piece is finished in shorter time

# RISC-V Pipelined Datapath


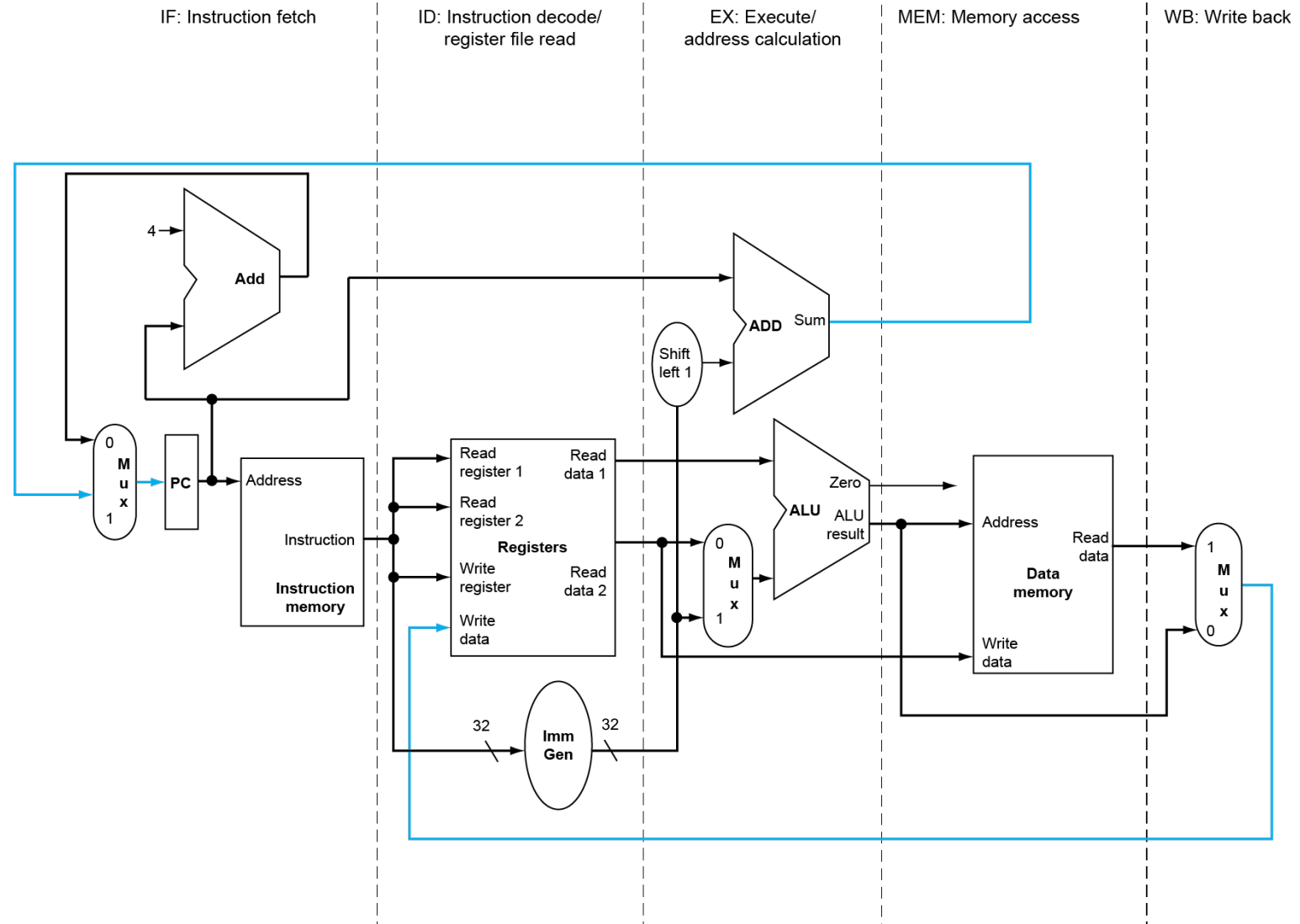


# RISC-V Pipeline

- Five stages, one step per stage per cycle
  1. IF: Instruction fetch from memory
  2. ID: Instruction decode & register read
  3. EX: Execute operation or calculate address
  4. MEM: Access memory operand
  5. WB: Write result back to register
  
# Pipelining Analogy

- Pipelined laundry: overlapping execution
  - Parallelism improves performance



- Four loads:


- Speedup  
 $= 8/3.5 = 2.3$

- Non-stop:

- Speedup  
 $\approx 2*n/0.5*n = 4$   
 $= \text{number of stages}$
  - $n$  is number of instructions
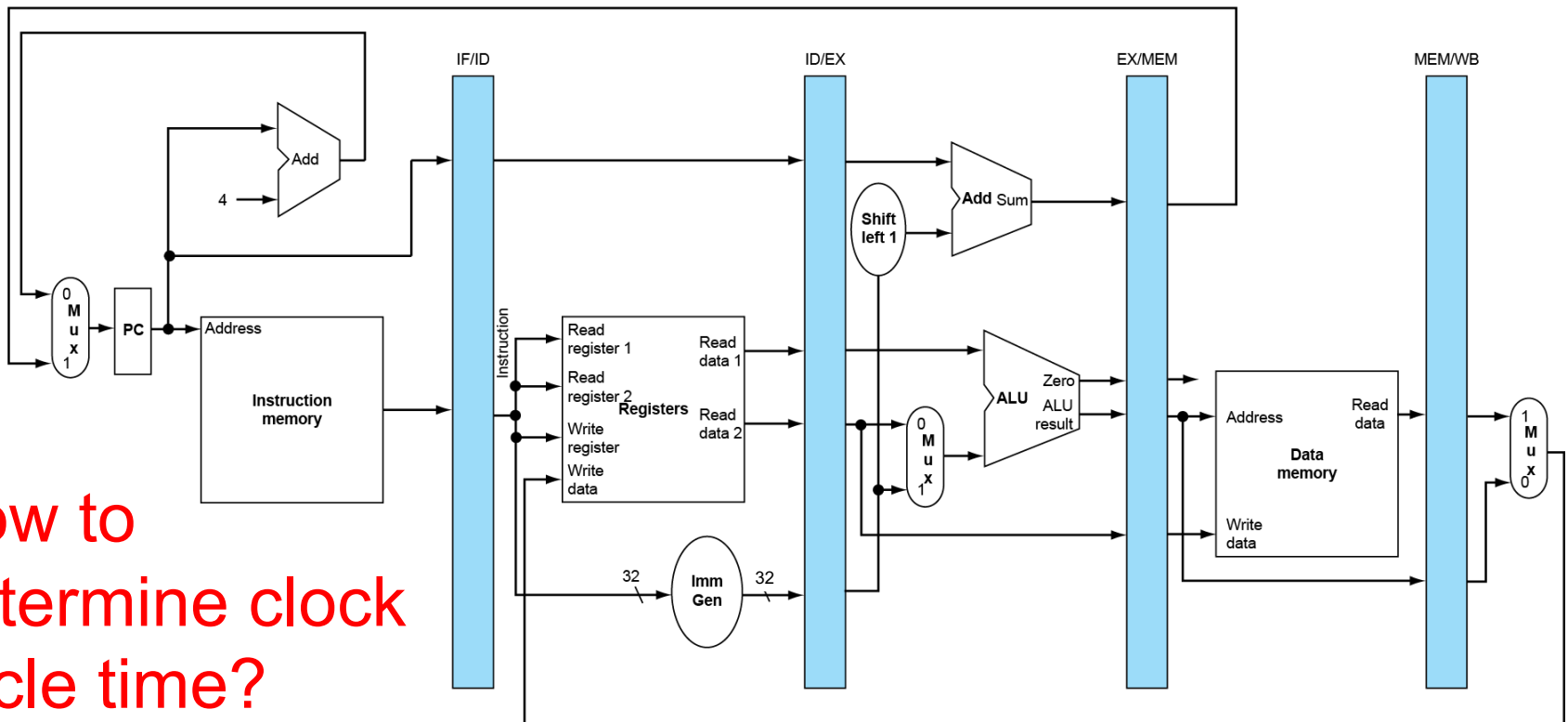
# Pipeline registers

- Need registers between stages
  - To hold information produced in previous cycle




How to  
determine clock  
cycle time?

# Recall the Shift Register
 
## ■ Implementation:

- Connect Q output of one flip flop to the D input of the next flip flop
- 4-bit shift register




	IN	OUT(3:0)
Initial value:	0	0110
rising edge:	0	0011
rising edge:	0	0001
rising edge:	0	0000
rising edge:	1	1000
rising edge:	0	0100

# Pipeline Operation


- Cycle-by-cycle flow of instructions through the pipelined datapath
- Representation/illustration:
  - “Single-clock-cycle” pipeline diagram
    - Shows pipeline usage in a single cycle
    - Highlight resources used
  - “multi-clock-cycle” pipeline diagram
    - Graph of operation over time

# IF for Load, Store, ...

 





# ID for Load, Store, ...

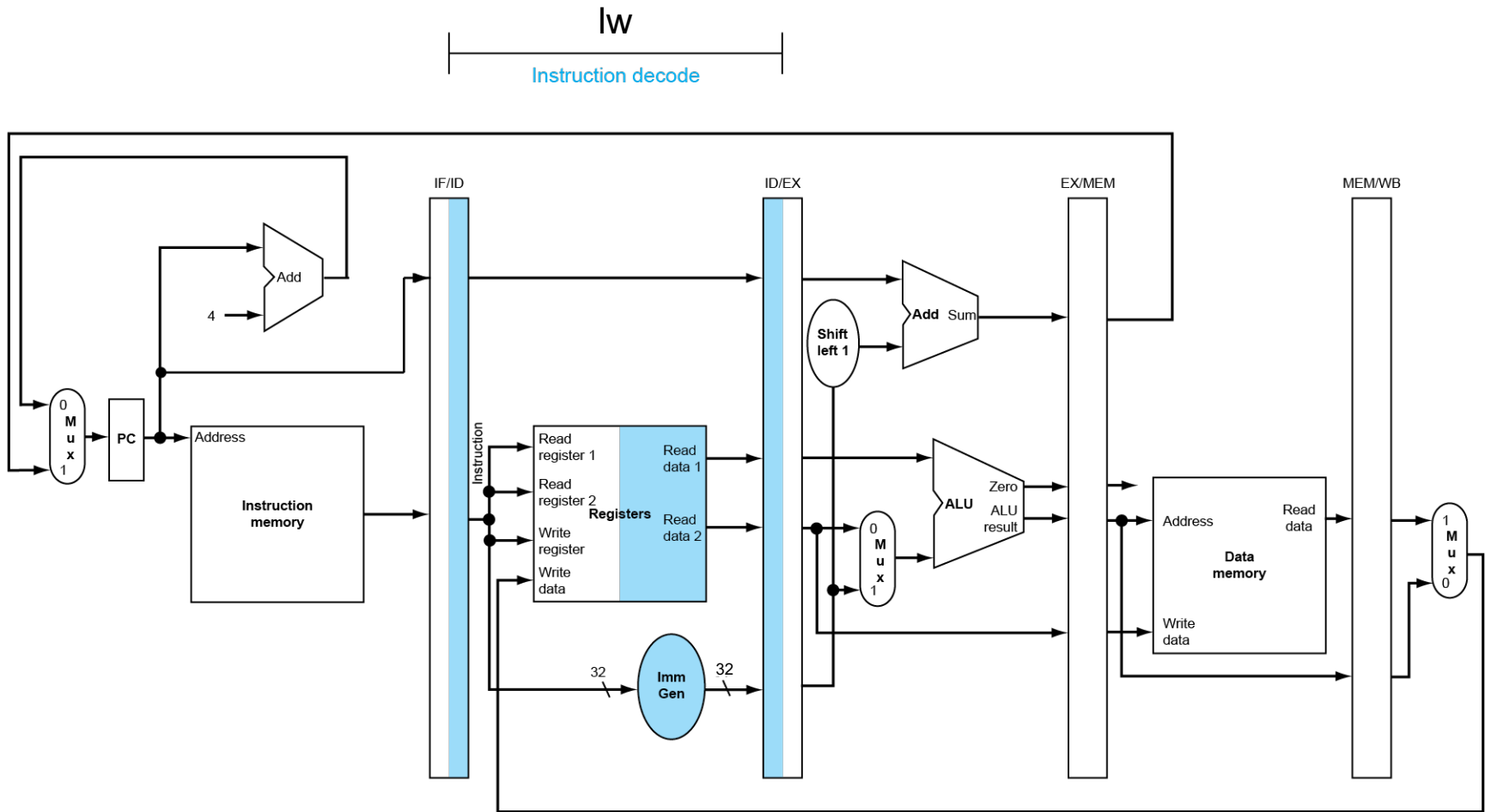


# EX for Load

 

# MEM for Load

 


# WB for Load

 

 
# Corrected Datapath for Load


- Pass alive signals along with the instruction through the pipeline
- Has to write/read register file at the same time
  - Writing reg in first half of clock
  - Reading reg in second half of clock



# EX for Store

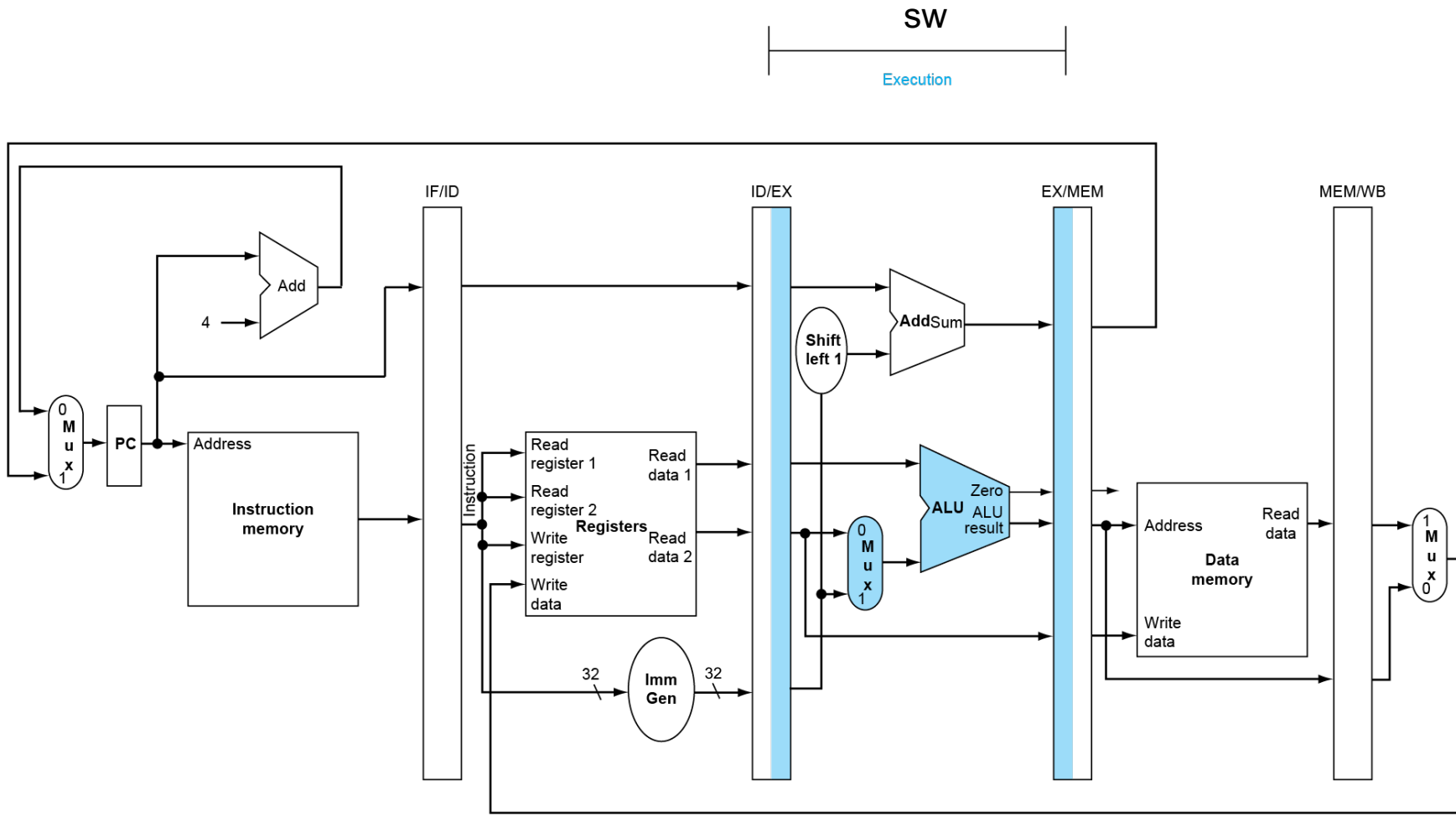


# MEM for Store

 

# WB for Store

No operation


Write-back

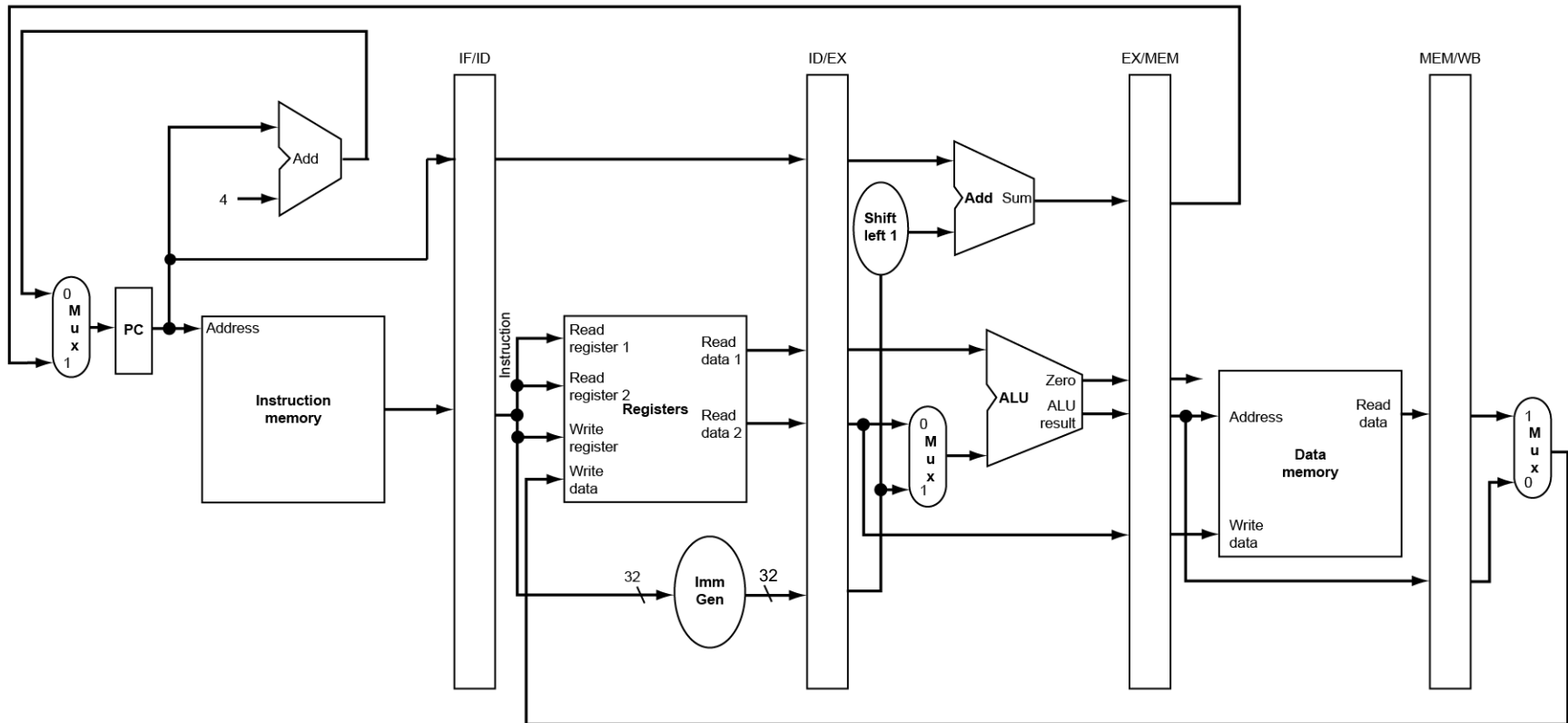



# Single-Cycle Pipeline Diagram


- State of pipeline in a given cycle

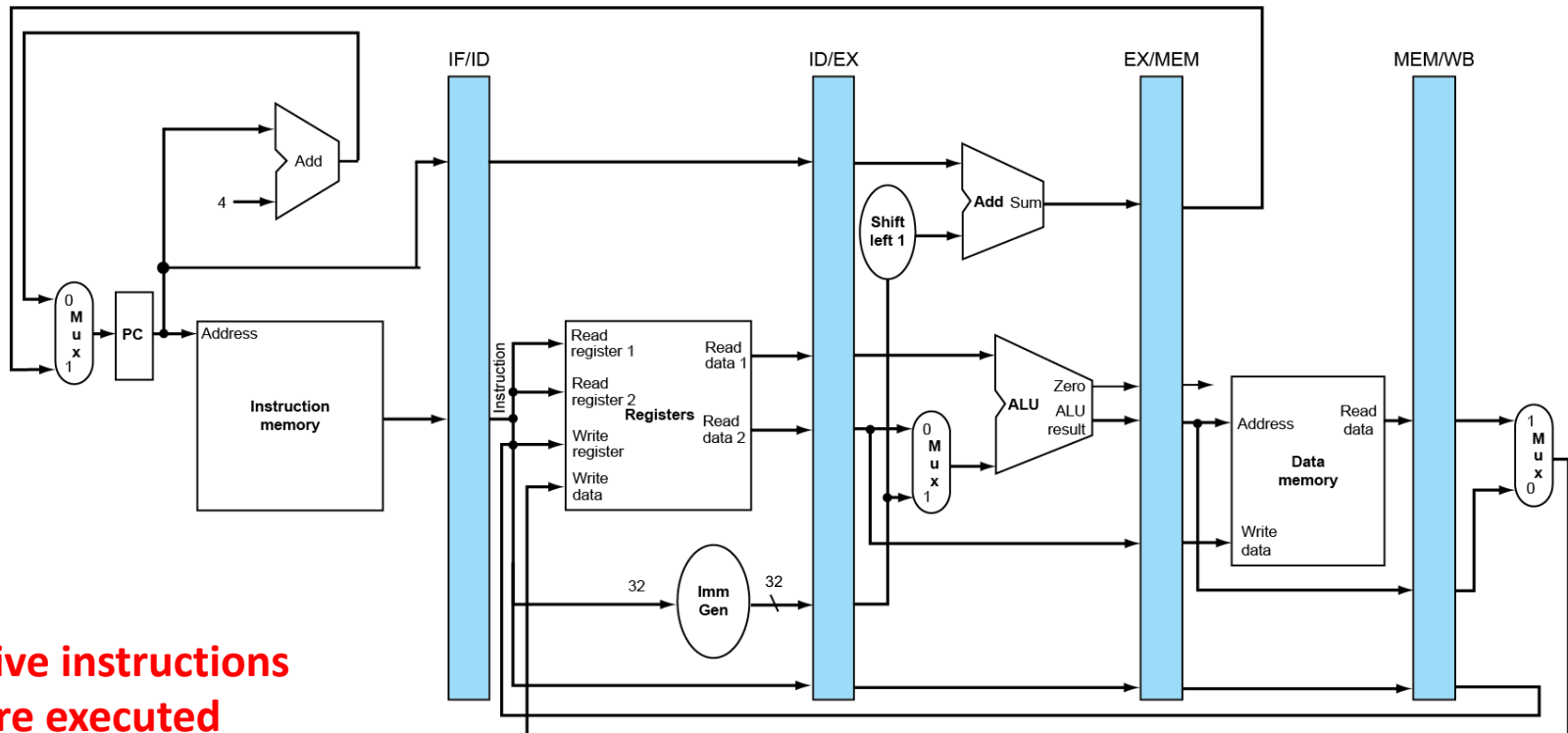

**Five instructions  
are executed  
concurrently!**


# Multi-Cycle Pipeline Diagram

## ■ Showing resource usage

 

# Multi-Cycle Pipeline Diagram

## ■ Excel style

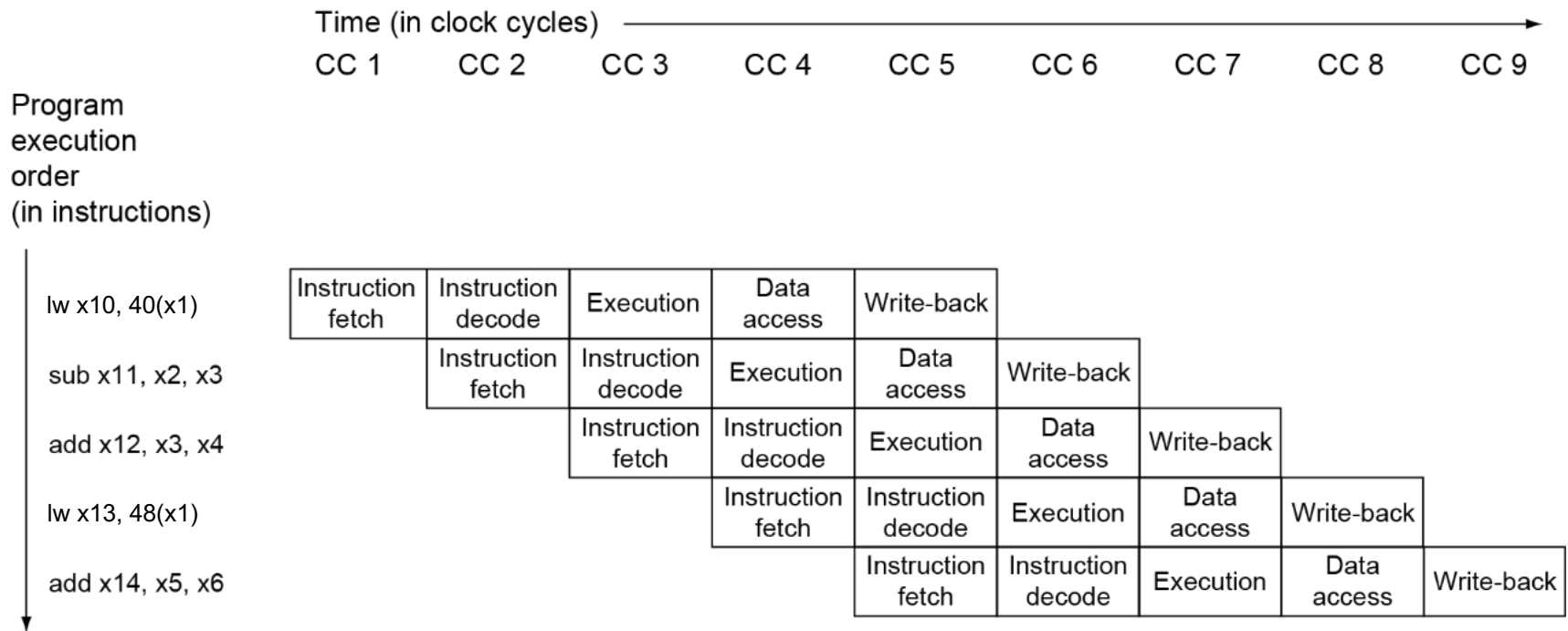



**How many clock cycles to execute these instructions?**

# Performance Consideration

- Assume time for stages is
  - 100ps for register read or write
  - 200ps for other stages
- Compare pipelined datapath with single-cycle and multi-cycle datapath

Instr	Instr fetch	Register read	ALU op	Memory access	Register write	Total time
lw	200ps	100 ps	200ps	200ps	100 ps	800ps
sw	200ps	100 ps	200ps	200ps		700ps
R-format	200ps	100 ps	200ps		100 ps	600ps
beq	200ps	100 ps	200ps			500ps

# Performance Consideration

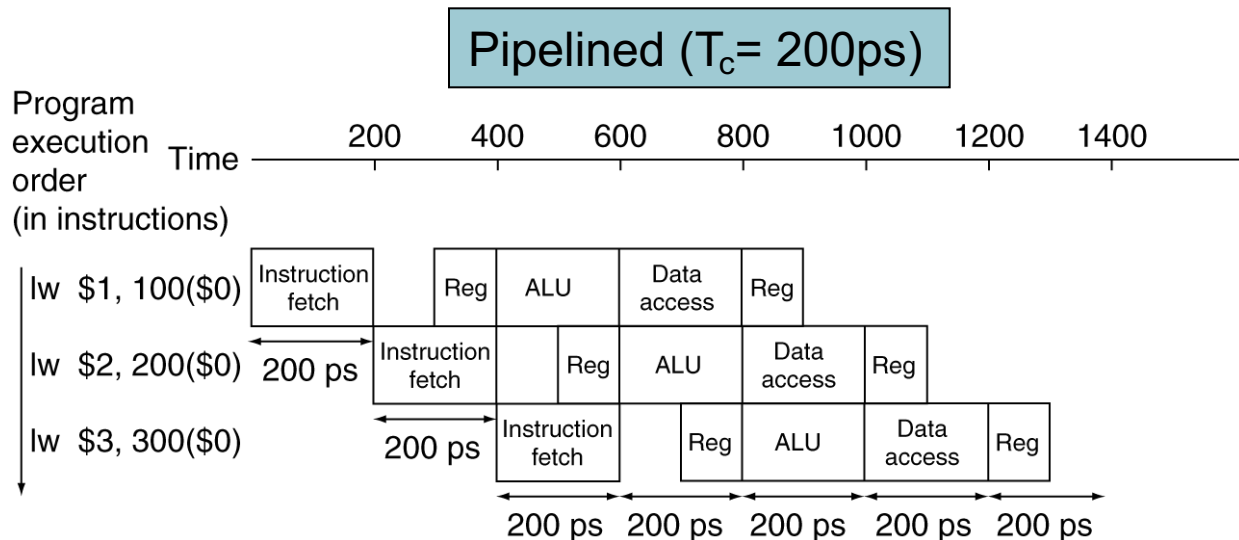 


# Performance Consideration

- Assume 100 instructions are executed
  - 30% are loads
  - 15% are stores
  - 40% are R format instructions
  - 15% are branches
- Execution time using pipelined processor?

# Pipeline Speedup

- If all stages are balanced
  - i.e., all take the same time
  - Time between instructions<sub>pipelined</sub>  
$$= \frac{\text{Time between instructions}_{\text{nonpipelined}}}{\text{Number of stages}}$$
- If not balanced (previous example),
  - Speedup is less
- Speedup due to increased throughput
  - Latency (time for each instruction) does not decrease


# Pipelined Control (Simplified)

 



 
# Pipelined Control


- Control signals derived from instruction
  - Passed along with corresponding instruction
  - Consumed in appropriate stages



# Pipelined Control

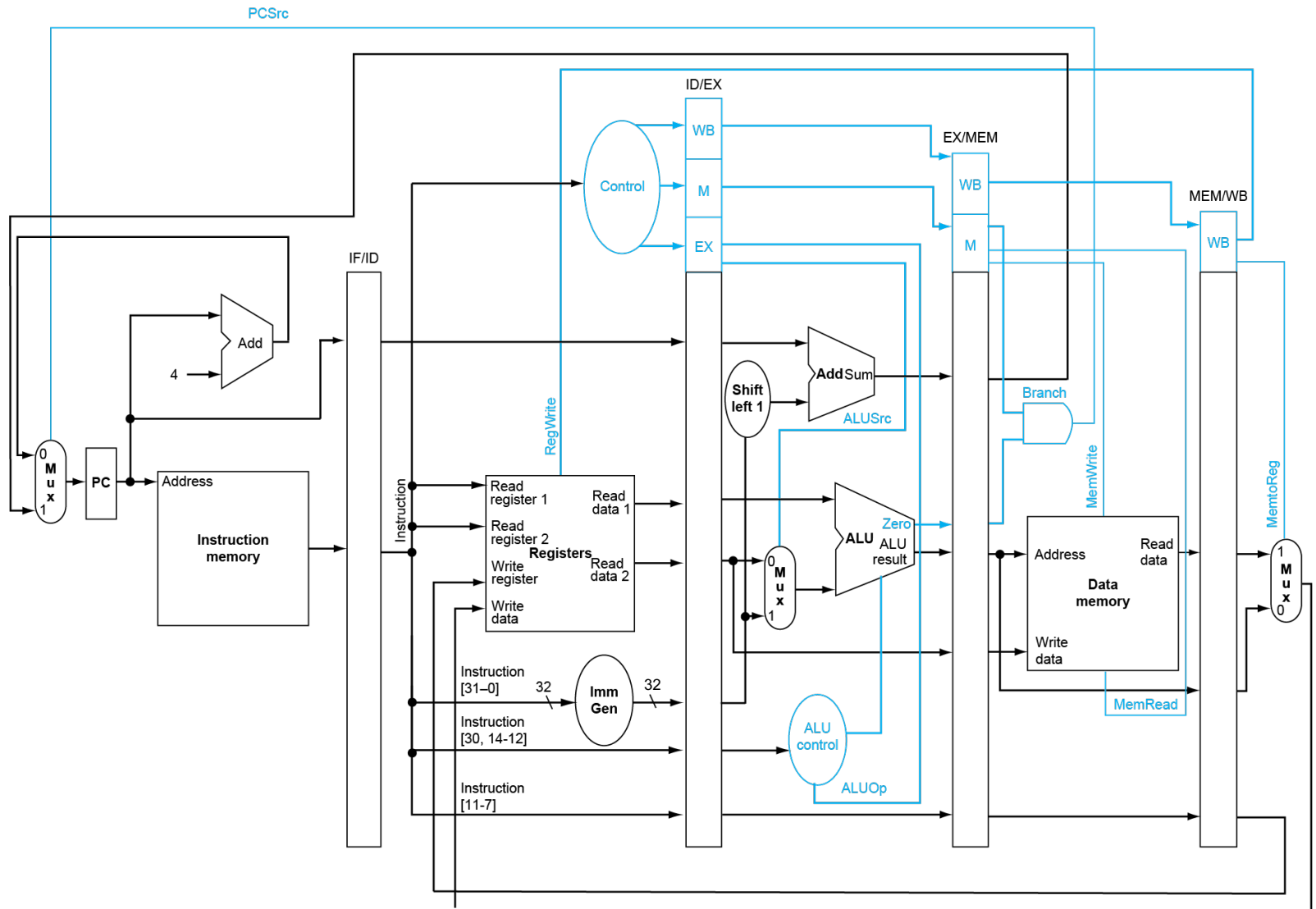


# What's happening in each stage?

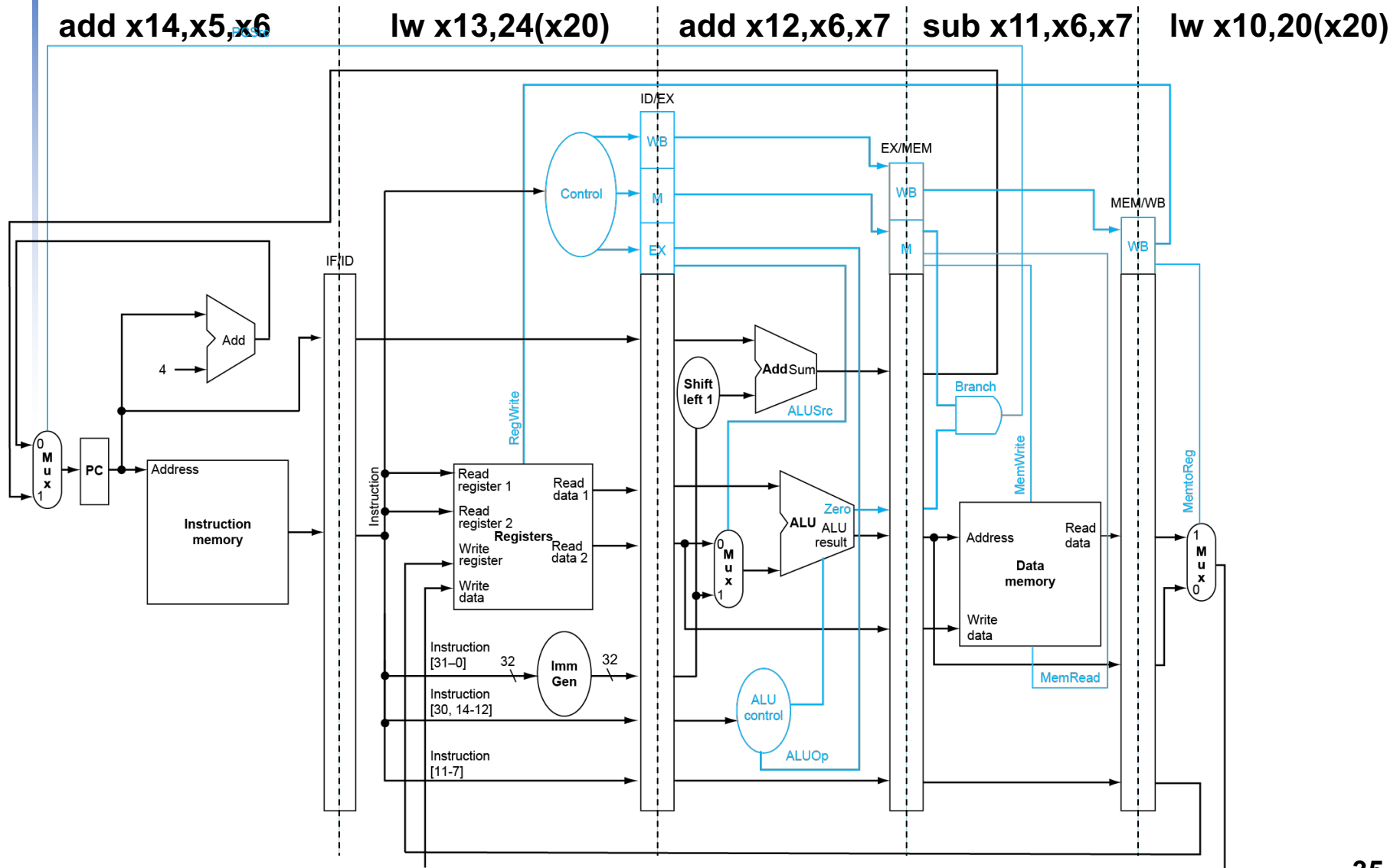


# ■ add x14, x5, x6 # IF

PC Src	PC	IM Output	MUX0	MUX1

 


# lw x13, 24(x20) # ID

Reg Write	Rd reg1	Rd reg2	Wr reg	Wr Data	Imm Gen out	rd	(1)

 


■ add x12, x6, x7 # EX

ALU Src	ADD A	ADD B	ALU MUX0	ALU MUX1	ALU A	ALU out	Zero	Mem Write	Mem Read
ALU Ctrl in	ALU Op	ALU Ctrl out	rd	Reg Write	MemtoReg	Branch			

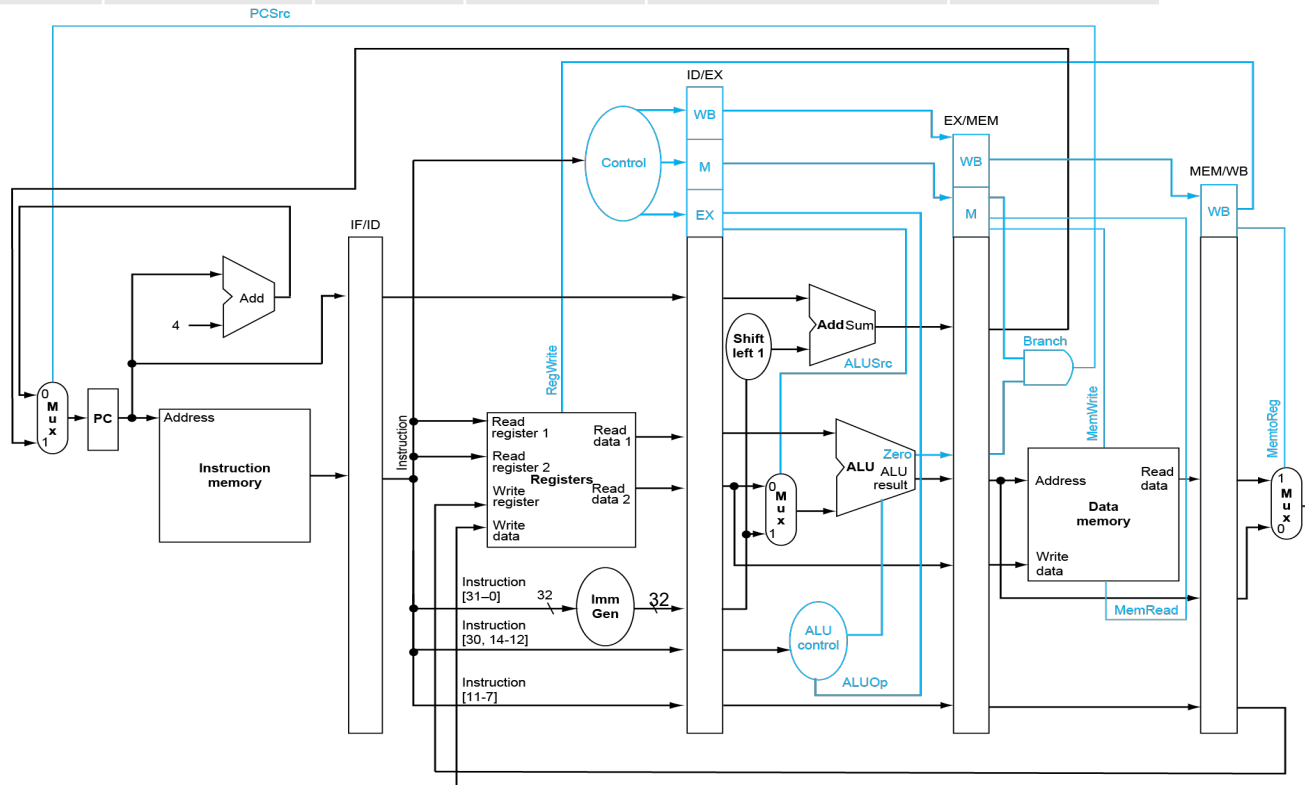


# ■ sub x11, x6, x7 # MEM

Addr	Write data	Read data	Mem Write	Mem Read	Zero	Branch	MemtoReg	Reg Write	(1)

 

# lw x10, 20(x20) # WB

MUX0	MUX1	Write register	Write data	MemtoReg	Reg Write

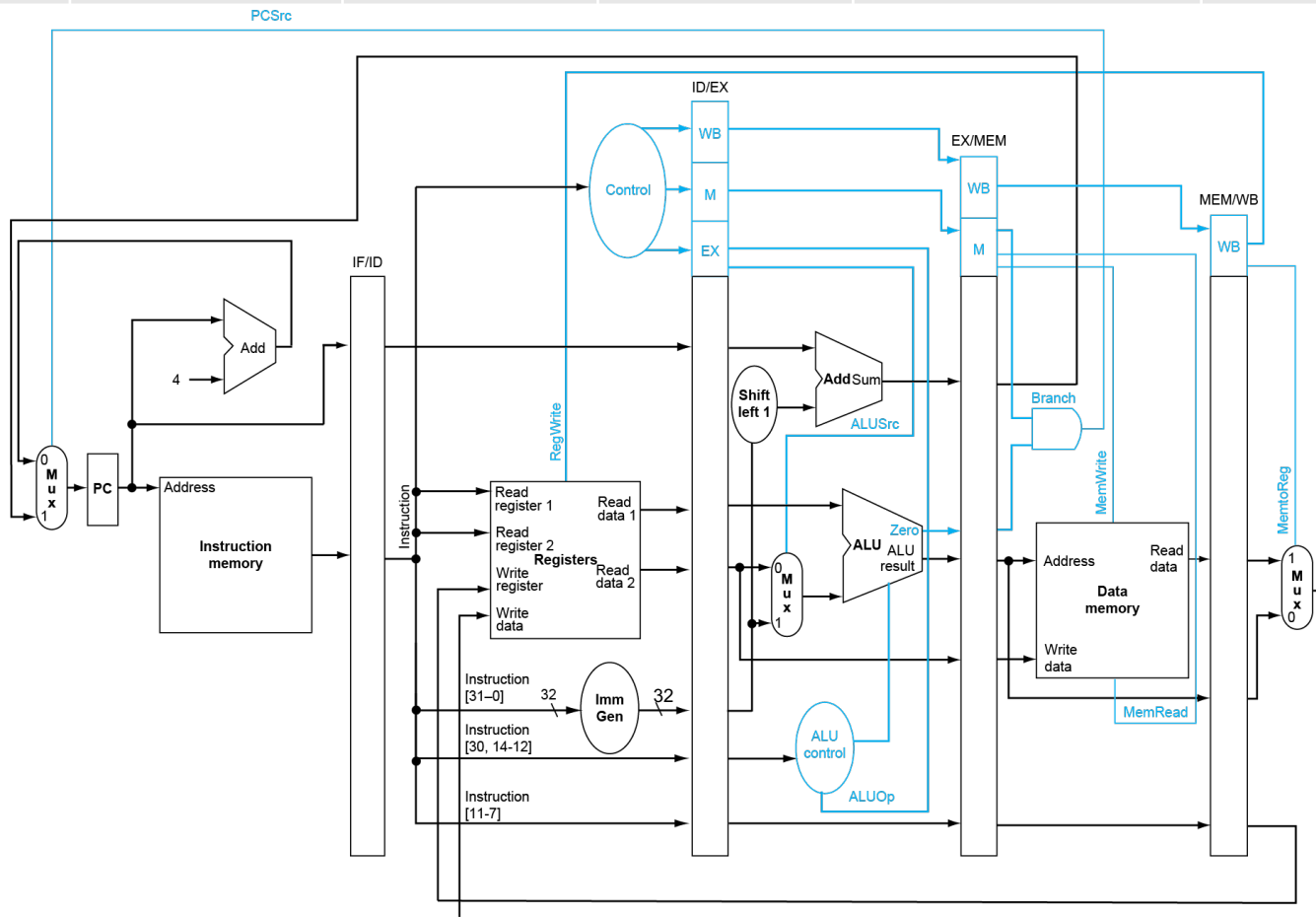



# Pipeline Summary

## The BIG Picture

- Pipelining improves performance by increasing instruction throughput
  - Executes multiple instructions in parallel
  - Each instruction has the same latency
- Subject to hazards
  - Structure, data, control
- Instruction set design affects complexity of pipeline implementation